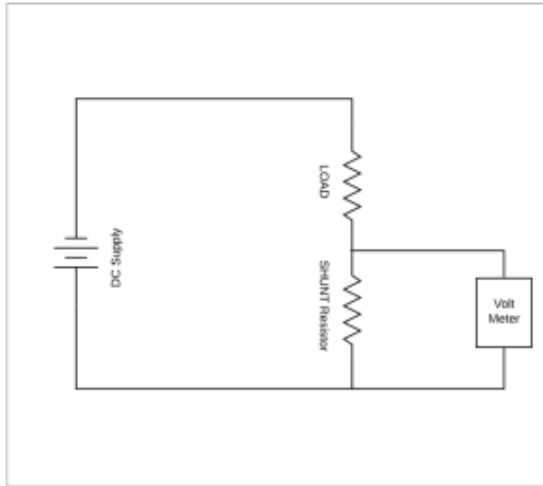


Current Measurement Using a Shunt

Today, practically every control and monitoring circuit uses shunt-based current measurements as an alternative to sensors. To make these measurements accurately, it is useful to understand how shunts work. Because the method is categorized as a precision measuring technology, it should not be regarded as trivial.

A shunt is a low-value resistor used to measure current – it is therefore also referred to as a current-sense resistor. The shunt typically connects in series so it carries the current of interest. A voltage measurement device then connects in parallel with the shunt. The current through the shunt generates a voltage drop that is measured. The current value is derived from Ohm's law and the known resistance ($I=V/R$). To keep power loss – and thus heat development – to a minimum, shunts must have resistive values no higher than the milliohm range. Some are even below that.



$$V=IR$$

$$I=V/R$$

Shunt Resistor:

- needs to be small such that it does not disrupt existing circuit.
- large enough to get a measurable voltage

Be careful about power rating.

$$P=I^2R$$

$$p=10^2 \times 10$$

$$= 1000w$$

Example Shunt for 12V :

Max Amp	50A
R	10
$I = V(\text{measured})/R$	$8v/10 = 0.8A$
$P=I^2R$	$=50^2 \times 10$ $=250 \text{ kw}$

References

Reference	URL
Measuring current with shunt resistors	https://www.powerelectronicstips.com/measuring-current-shunt-resistors/