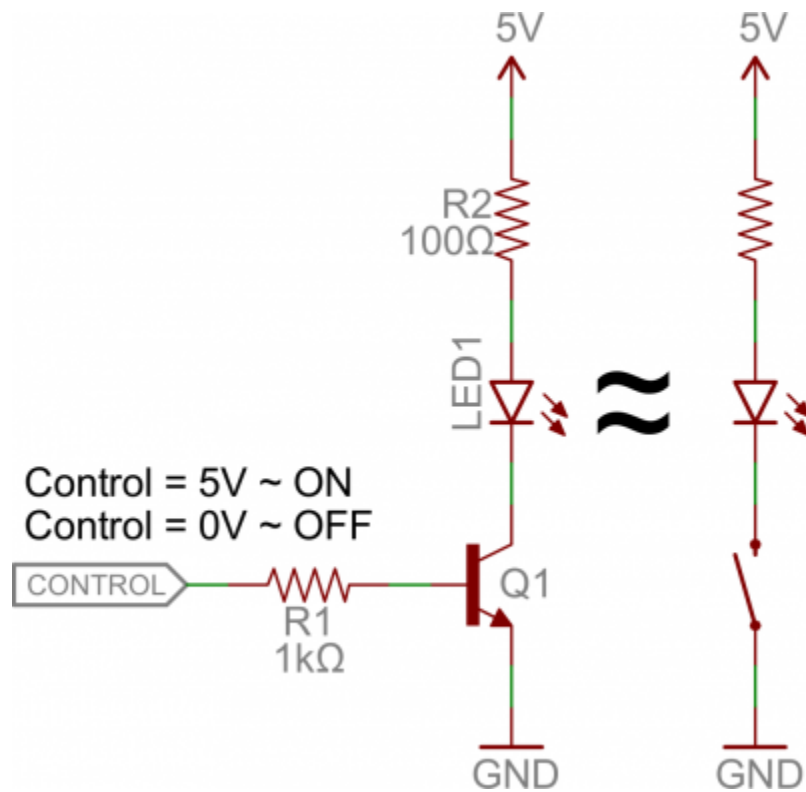


# Transistors as a Switch

Let's look at the most fundamental transistor-switch circuit: an NPN switch. Here we use an NPN to control a high-power LED:




Our control input flows into the base, the output is tied to the collector, and the emitter is kept at a fixed voltage.

While a [normal switch](#) would require an actuator to be physically flipped, this switch is controlled by the voltage at the base pin. A microcontroller I/O pin, like those on an [Arduino](#), can be programmed to go high or low to turn the LED on or off.

When the voltage at the base is greater than 0.6V (or whatever your transistor's  $V_{th}$  might be), the transistor starts saturating and looks like a short circuit between collector and emitter. When the voltage at the base is less than 0.6V the transistor is in cutoff mode – no current flows because it looks like an open circuit between C and E.

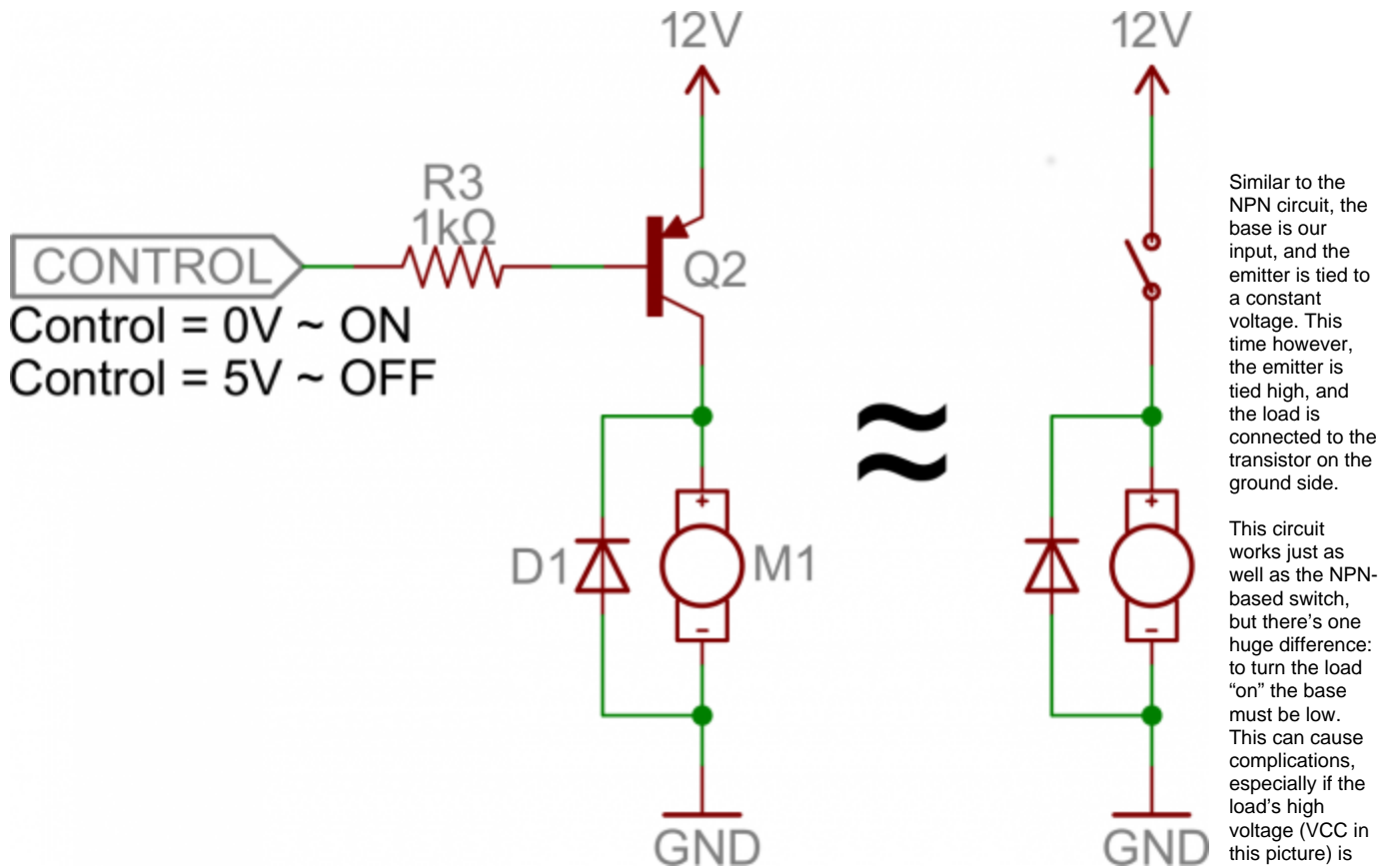The circuit above is called a low-side switch, because the switch – our transistor – is on the low (ground) side of the circuit. Alternatively, we can use a PNP transistor to create a high-side switch:




control input's high voltage. For example, this circuit wouldn't work if you were trying to use a 5V-operating Arduino to switch on a 12V motor. In that case it'd be impossible to turn the switch off because  $V_B$  would always be less than  $V_E$ .


### Base Resistors!

You'll notice that each of those circuits uses a series resistor between the control input and the base of the transistor. Don't forget to add this resistor! A transistor without a resistor on the base is like an LED with no [current-limiting resistor](#).

Recall that, in a way, a transistor is just a pair of interconnected diodes. We're forward-biasing the base-emitter diode to turn the load on. The diode only needs 0.6V to turn on, more voltage than that means more current. Some transistors may only be rated for a maximum of 10-100mA of current to flow through them. If you supply a current over the maximum rating, the transistor might blow up.

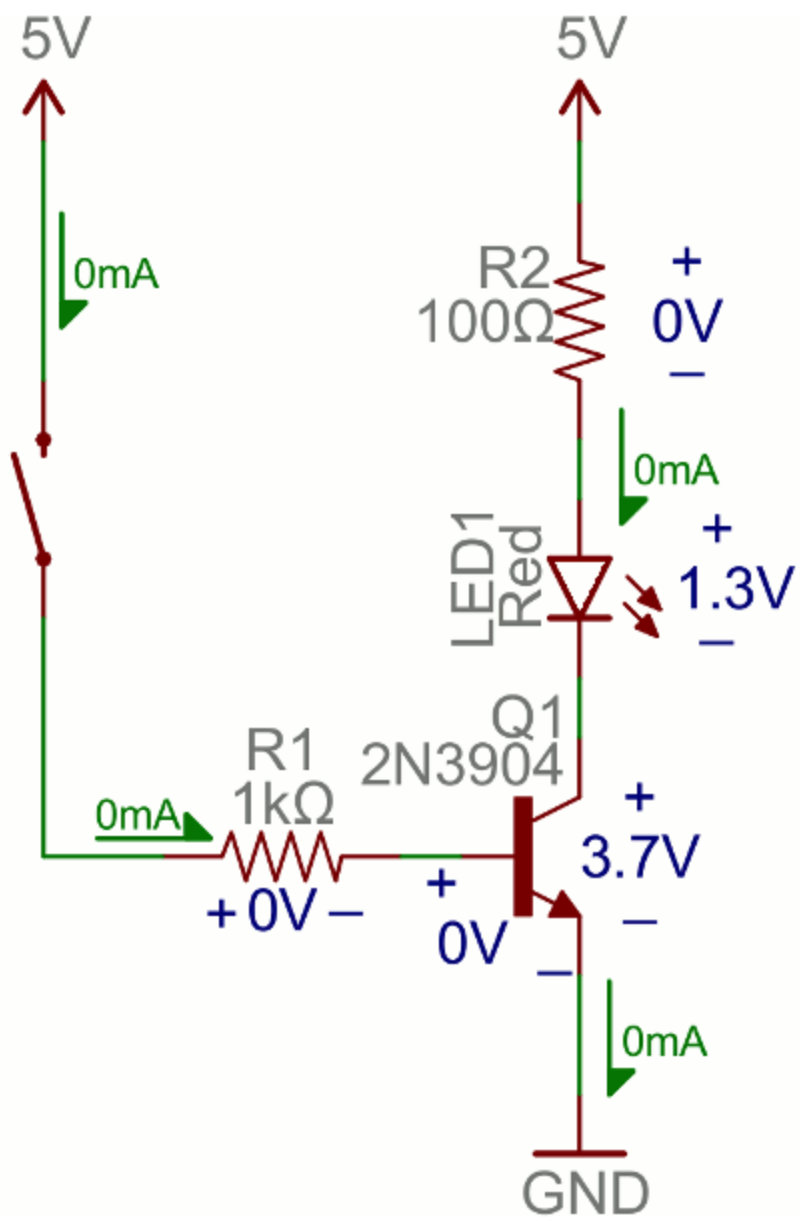The series resistor between our control source and the base limits current into the base. The base-emitter node can get its happy voltage drop of 0.6V, and the resistor can drop the remaining voltage. The value of the resistor, and voltage across it, will set the current.



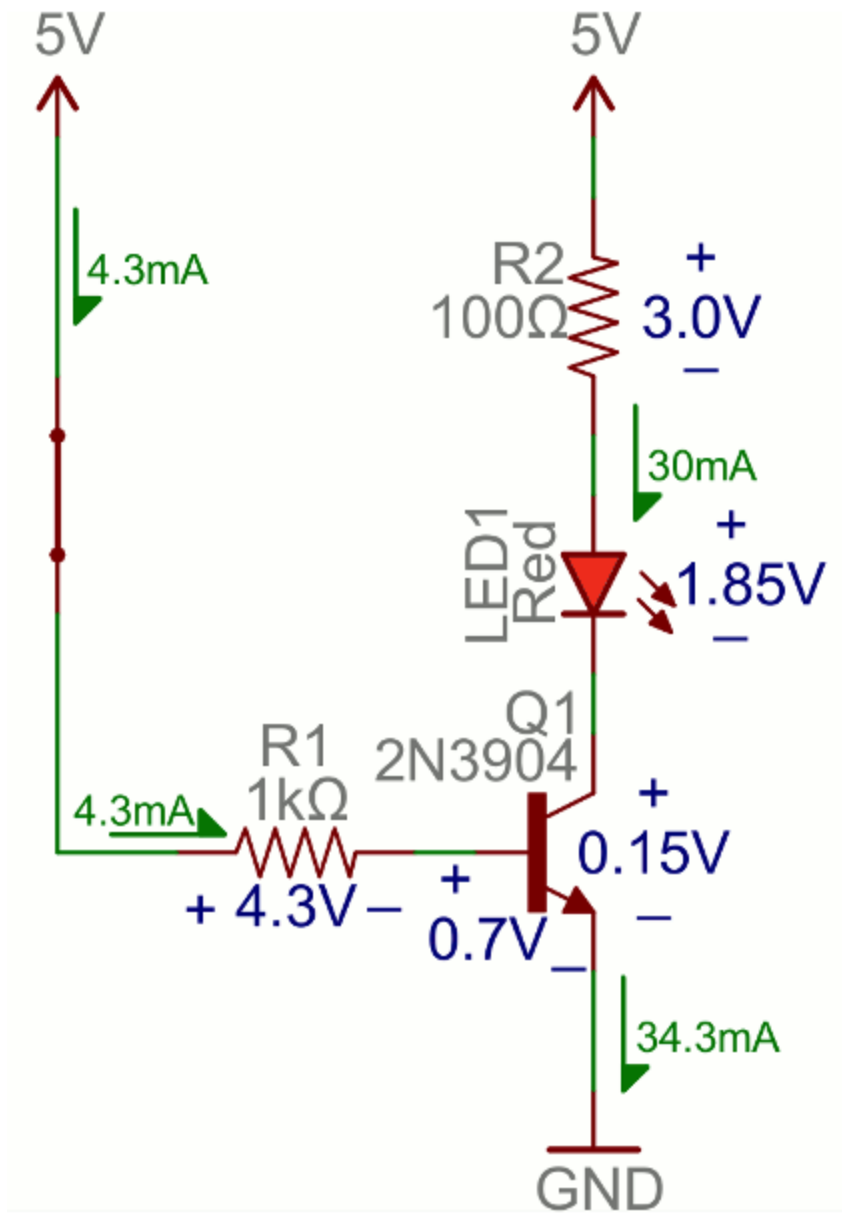

The resistor needs to be large enough to effectively *limit* the current, but small enough to feed the base *enough* current. 1mA to 10mA will usually be enough, but check your transistor's datasheet to make sure.

## References

Reference	URL
Transistors as a Switch	<a href="https://learn.sparkfun.com/tutorials/transistors/applications-i-switches">https://learn.sparkfun.com/tutorials/transistors/applications-i-switches</a>

