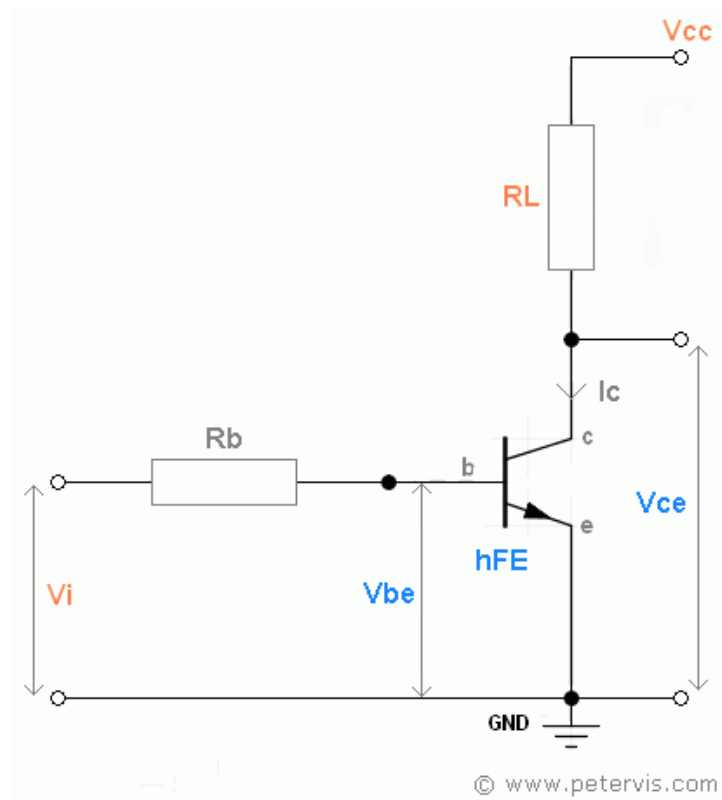


Transistors - Calculating Base Resistor for Switching

Overview


We will calculate the value of R_b based on the following circuit:



Questions to Ask when Sizing

- Can your transistor handle the load through the collector? Does it exceed $I_{c(max)}$?
- Can the transistor handle supply voltage? $V_{cc} > V_{ce(max)}$?
- Find the worst case current gain during saturation. I_c
- Calculate the minimum base current. I_b
- **Compare base current I_b max current your micro controller can deliver.**
- Find worst case (highest) V_{be}
- Calculate voltage drop across base resistor using V_{be} and micro controller output
- Calculate required base resistor R_b .
- Calculate collector power dissipation.

Calculating the R_b Value

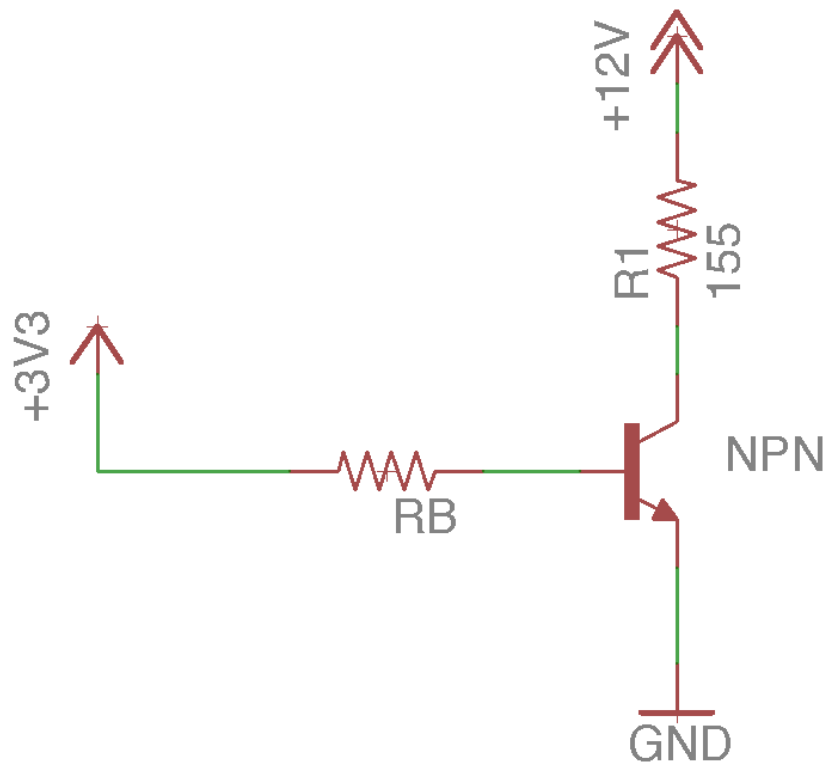

Precondition	Value
Vcc	12v
Vi	3.3v
RL	155
NPN BC337	
Vbe(sat)	1.2v
Vce(sat)	0.7v
hFE (@100mA)	100

Calculations for Ic:

$$I_c = (V_{cc} - V_{ce}) / R_L = 11.3v / 155 = 73 \text{ mA}$$

Calculation for Vb

$$V_b = V_i - V_{be(sat)} = 3.3 - 1.2 = 2.1v$$

Calculating using $I_b = I_c / 10$ (** Best Approach)

It is common to assume that base current is 1/10 of the collector current.

$$I_b = I_c / 10 = 73 / 10 = 7.3 \text{ mA}$$

$$R_b = V_b / I_b = 2.1 / 0.0073 = 288$$

Confirm: Can the micro controller deliver Ib current required?

Tested with 220 and it worked.

Calculating using hFE

To guarantee that the transistor operates in the saturation region, we multiply the base current by a factor of three.

$hFE=100$ (@100mA)

$I_b = I_c/hFE = 73/100 = 0.73mA$

$R_b = V_b/I_b \times 3 = 2.1/(0.00073 \times 3) = 959$

This would be the max value for Rb.

Calculating using the online calculator

$hFE=100$

$R_b = 960$

This would be the max value for Rb.

Formulas

$I_c = (V - V_{ce})/R_L$

$I_b = I_c/hFE$

$R_b = (V_i - V_{be})/(3 \times I_b)$

References

Reference	URL
Base Resistor Calculator	https://www.petervis.com/GCSE_Design_and_Technology_Electronic_Products/transistor_base_resistor_calculator/transistor_base_resistor_calculator.html
Discussion Forum	https://forum.allaboutcircuits.com/threads/calculating-base-resistor-for-transistor.78483/